







## **Second Order Circuits**

---
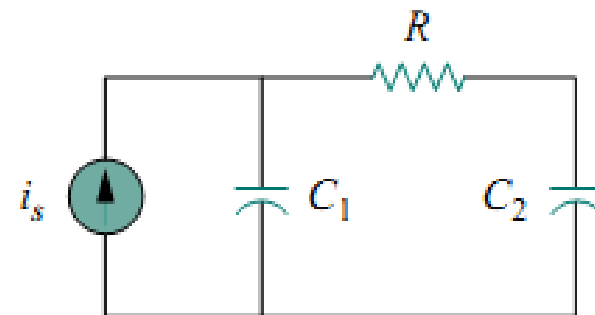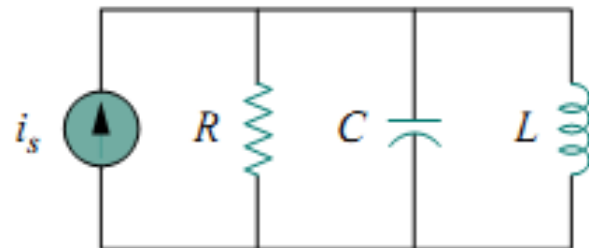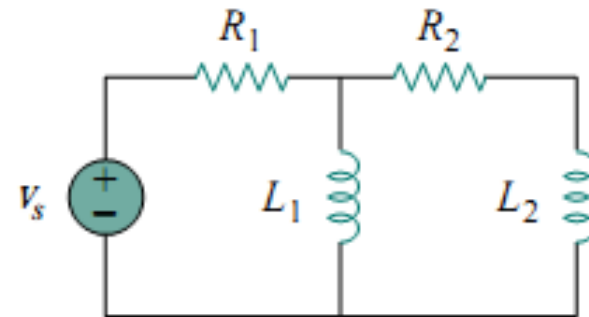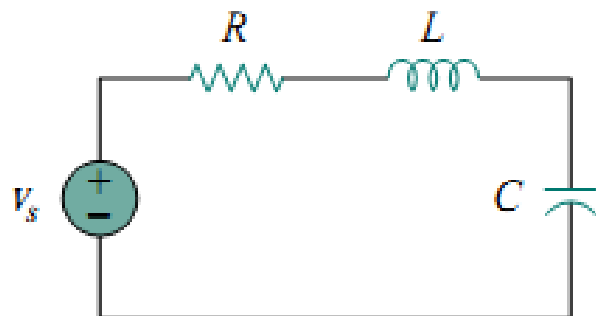
## Introduction


A second-order circuit is characterized by a second-order differential equation. It consists of resistors and the equivalent of two energy storage elements.




## Response of RLC Circuits

The complete response of the circuit is the sum of the natural response and the forced response.

$$x(t) = x_f(t) + x_n(t)$$

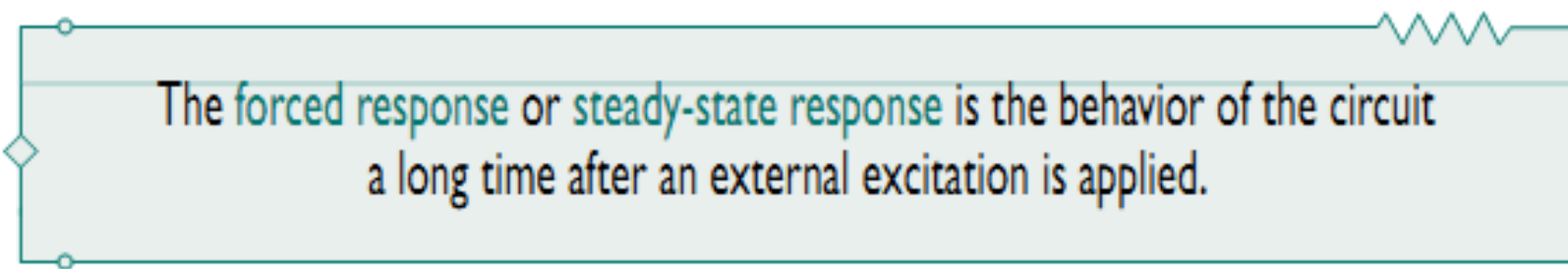

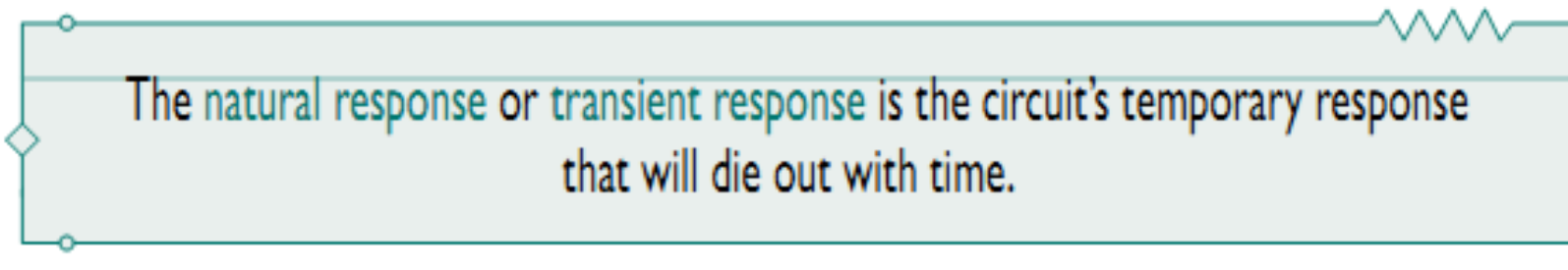
The forced response or steady-state response is the behavior of the circuit a long time after an external excitation is applied.



The natural response or transient response is the circuit's temporary response that will die out with time.

# The Natural Response


Series RLC Circuit

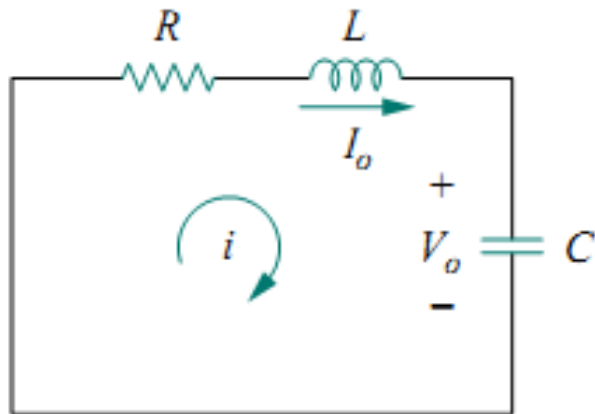

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i \, dt = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

Parallel RLC Circuit

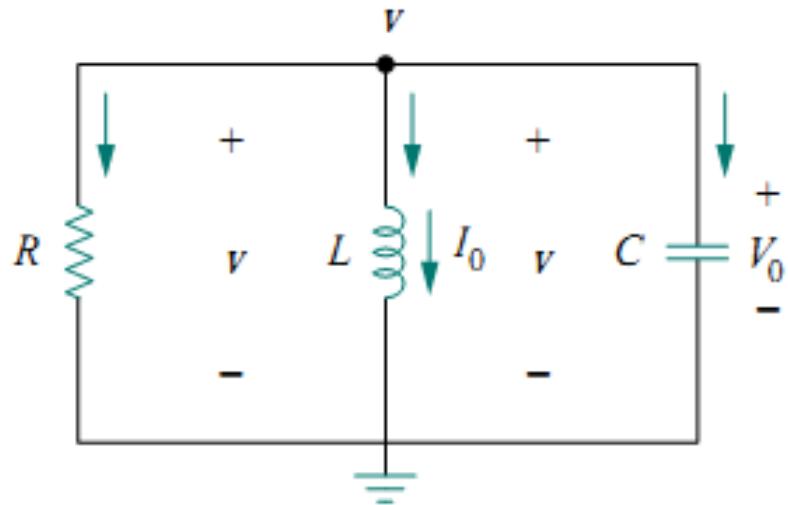

$$\frac{v}{R} + \frac{1}{L} \int_{-\infty}^t v \, dt + C \frac{dv}{dt} = 0$$

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

## General Equation

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$\frac{d^2 x}{dt^2} + 2\alpha \frac{dx}{dt} + \omega_0^2 x = 0$$

Series RLC Circuit

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Parallel RLC Circuit

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

## General Solution

### Overdamped Case ( $\alpha > \omega_0$ )

$$x = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\frac{dx}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

### Critically Damped Case ( $\alpha = \omega_0$ )

$$x = e^{-\alpha t} (A_1 t + A_2)$$

$$\frac{dx}{dt} = e^{-\alpha t} (A_1 - \alpha(A_1 t + A_2))$$


### Underdamped Case ( $\alpha < \omega_0$ )

$$x = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$

$$\frac{dx}{dt} = e^{-\alpha t} ((A_2 \omega_d - A_1 \alpha) \cos \omega_d t - (A_1 \omega_d + A_2 \alpha) \sin \omega_d t)$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

## Finding Initial Values

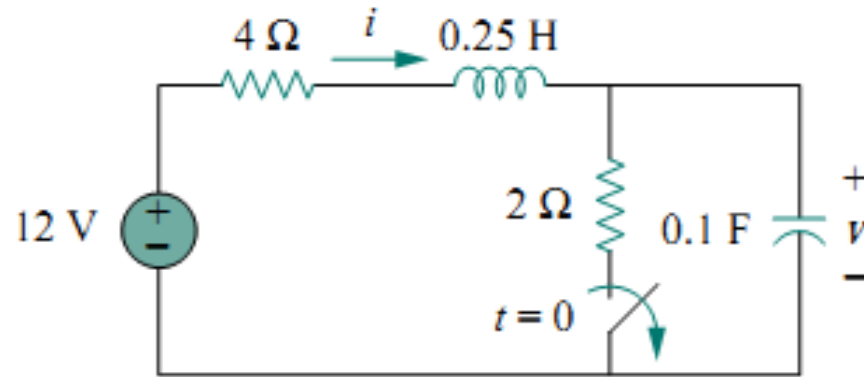


Find: (a)  $i(0^+)$ ,  $v(0^+)$ , (b)  $di(0^+)/dt$ ,  $dv(0^+)/dt$ .

The capacitor voltage is always continuous  $\Rightarrow v(0^+) = v(0^-)$


The inductor current is always continuous  $\Rightarrow i(0^+) = i(0^-)$

## Equivalent circuit

$t = 0^-$

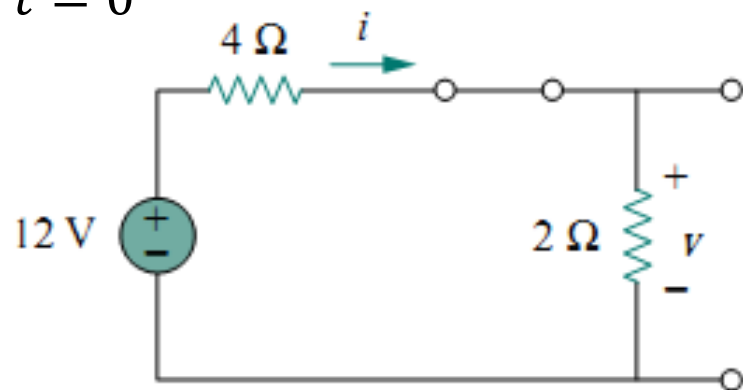


$t = 0^+$

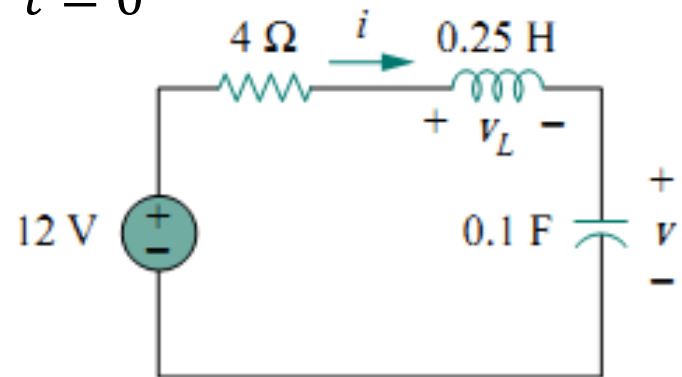



$t = 0^-$

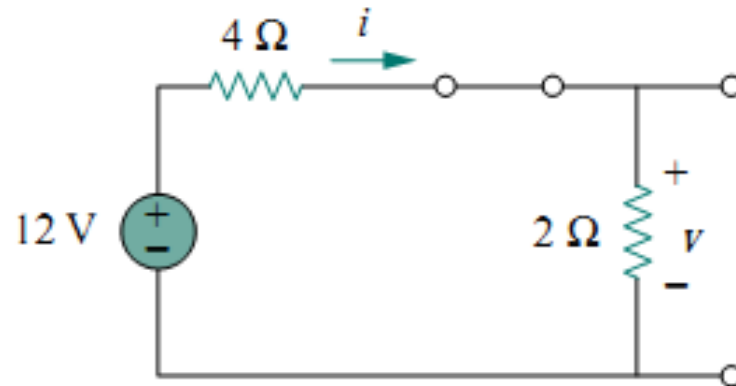


$$i(0^-) = \frac{12}{4 + 2} = 2\text{ A}, \quad v(0^-) = 2i(0^-) = 4\text{ V}$$

As the inductor current and the capacitor voltage cannot change abruptly

$$i(0^+) = i(0^-) = 2\text{ A}, \quad v(0^+) = v(0^-) = 4\text{ V}$$

$t = 0^+$

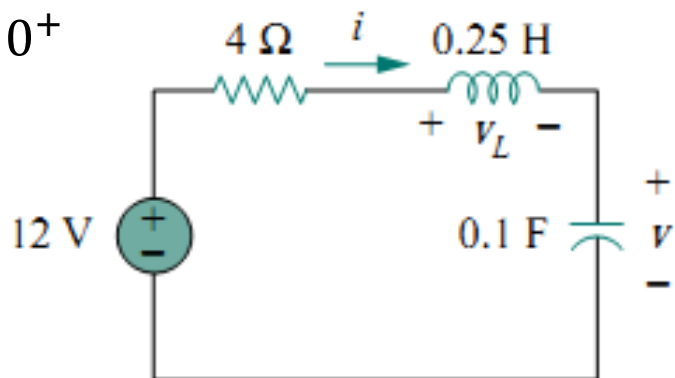

The same current flows through both the inductor and capacitor

$$i_C(0^+) = i(0^+) = 2\text{ A}$$

$$C \, dv/dt = i_C, \, dv/dt = i_C/C,$$



$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{2}{0.1} = 20\text{ V/s}$$

$$L \, di/dt = v_L, \, di/dt = v_L/L$$




$$-12 + 4i(0^+) + v_L(0^+) + v(0^+) = 0$$

$$v_L(0^+) = 12 - 8 - 4 = 0$$


$$\frac{di(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{0}{0.25} = 0\text{ A/s}$$

## Example

- 1 Find  $i(t)$  for  $t > 0$

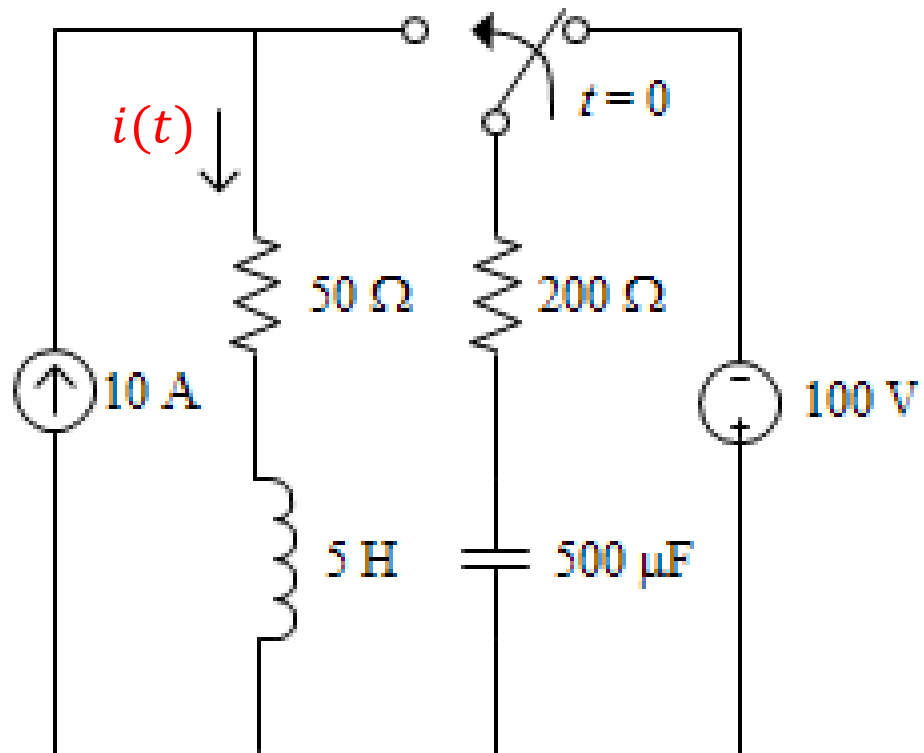

## The forced response

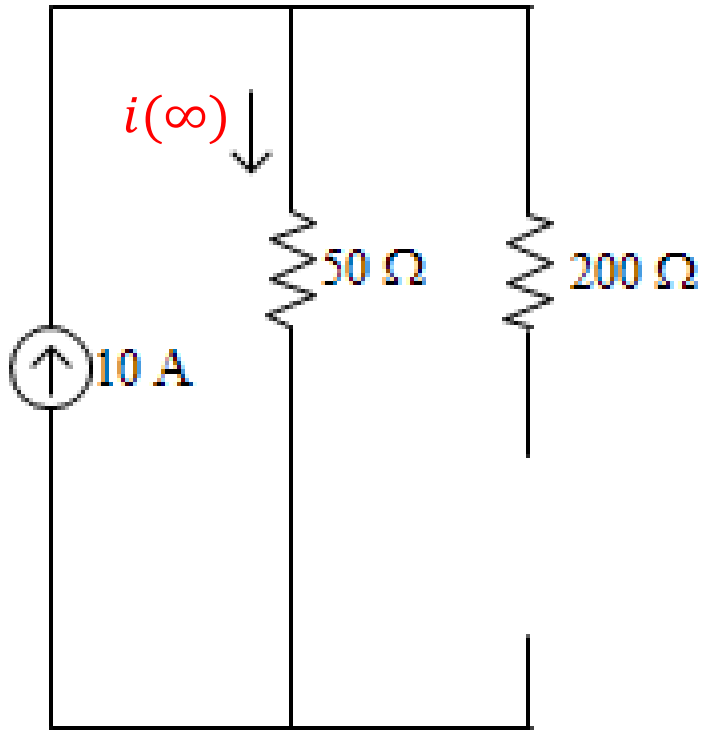

$$t \rightarrow \infty$$

$$i(\infty) = 10 \text{ A}$$

$$i_f(t) = i(\infty) = 10 \text{ A}$$

## The natural response

$$\alpha = \frac{R}{2L} = \frac{(200 + 50)}{2(5)} = 25$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5(500 \cdot 10^{-6})}} = \frac{100}{5} = 20$$

$$\alpha > \omega_0 \Rightarrow \text{Overdamped}$$


$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -25 \pm \sqrt{625 - 400} = -25 \pm 15$$

$$s_1 = -10 \quad s_2 = -40$$

$$i_n(t) = A_1 e^{-10t} + A_2 e^{-40t} \text{ A}$$

## The initial values

$$t = 0^-$$

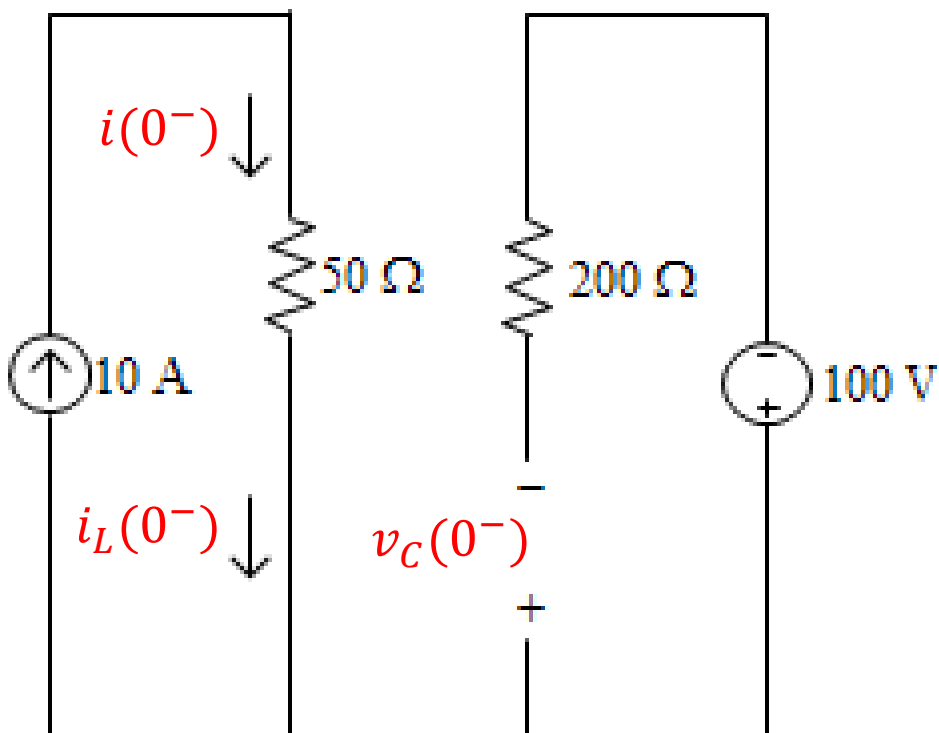


$$i(0^-) = 10\text{ A}$$

$$i_L(0^-) = i(0^-) = 10\text{ A}$$

$$v_C(0^-) = 100\text{ V}$$

$$t = 0^+$$

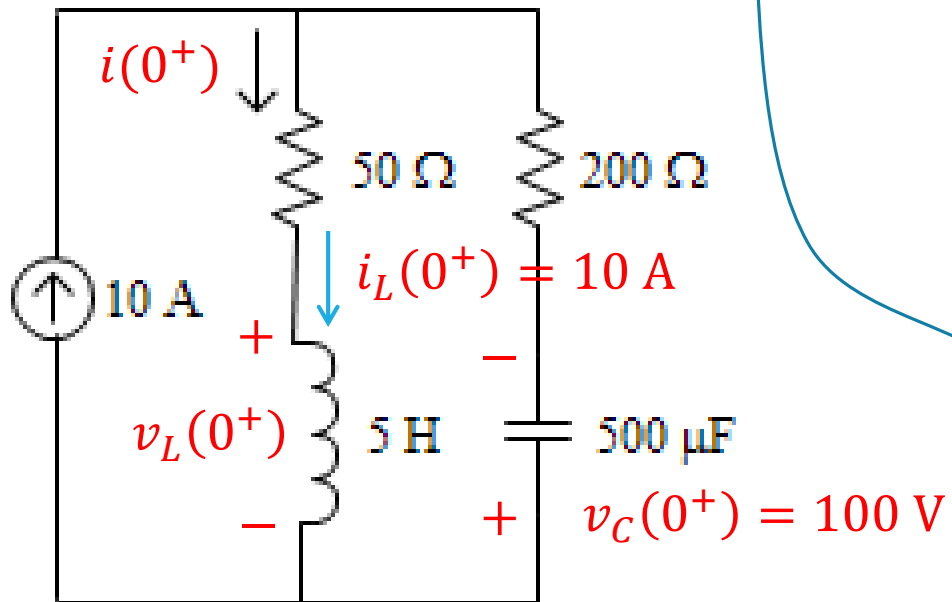


$$i_L(0^+) = i_L(0^-) = 10\text{ A}$$

$$v_C(0^+) = v_C(0^-) = 100\text{ V}$$

$$i(0^+) = i_L(0^+) = 10\text{ A}$$
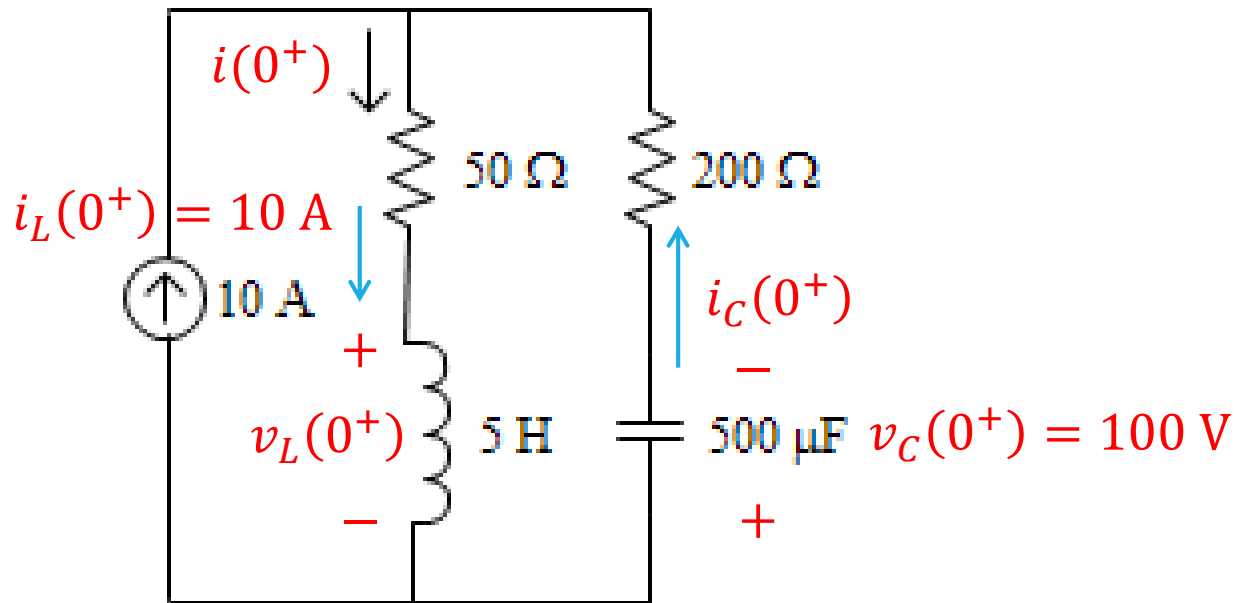
$$\frac{di(0^+)}{dt} = \frac{di_L(0^+)}{dt} = \frac{v_L(0^+)}{L}$$



$$50 i(0^+) + v_L(0^+) + v_C(0^+) + 200 i_C(0^+) = 0$$

$$50 (10) + v_L(0^+) + 100 + 200 (0) = 0$$

$$v_L(0^+) = -600 \text{ V}$$

$$\frac{di(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{-600}{5}$$

$$\frac{di(0^+)}{dt} = -120 \text{ A/s}$$



## The complete response

$$i(t) = i_f(t) + i_n(t)$$

$$i(t) = 10 + A_1 e^{-10t} + A_2 e^{-40t} \text{ A}$$

$$\frac{di(t)}{dt} = -10 A_1 e^{-10t} - 40 A_2 e^{-40t} \text{ A/s}$$

$$t = 0^+$$

$$i(0^+) = 10 + A_1 + A_2$$

$$10 = 10 + A_1 + A_2$$

$$\frac{di(0^+)}{dt} = -10 A_1 - 40 A_2$$

$$-120 = -10 A_1 - 40 A_2$$

$$A_1 + A_2 = 0 \quad (1)$$

$$A_1 + 4 A_2 = 12 \quad (2)$$

From equation (1) and (2) :  $A_1 = -4$   $A_2 = 4$

$$i(t) = 10 - 4 e^{-10t} + 4 e^{-40t} \text{ A} \quad (t > 0)$$

**The additional note**

$$i(t) = \begin{cases} 10 \text{ A} & t < 0 \\ 10 - 4 e^{-10t} + 4 e^{-40t} \text{ A} & t > 0 \end{cases}$$

